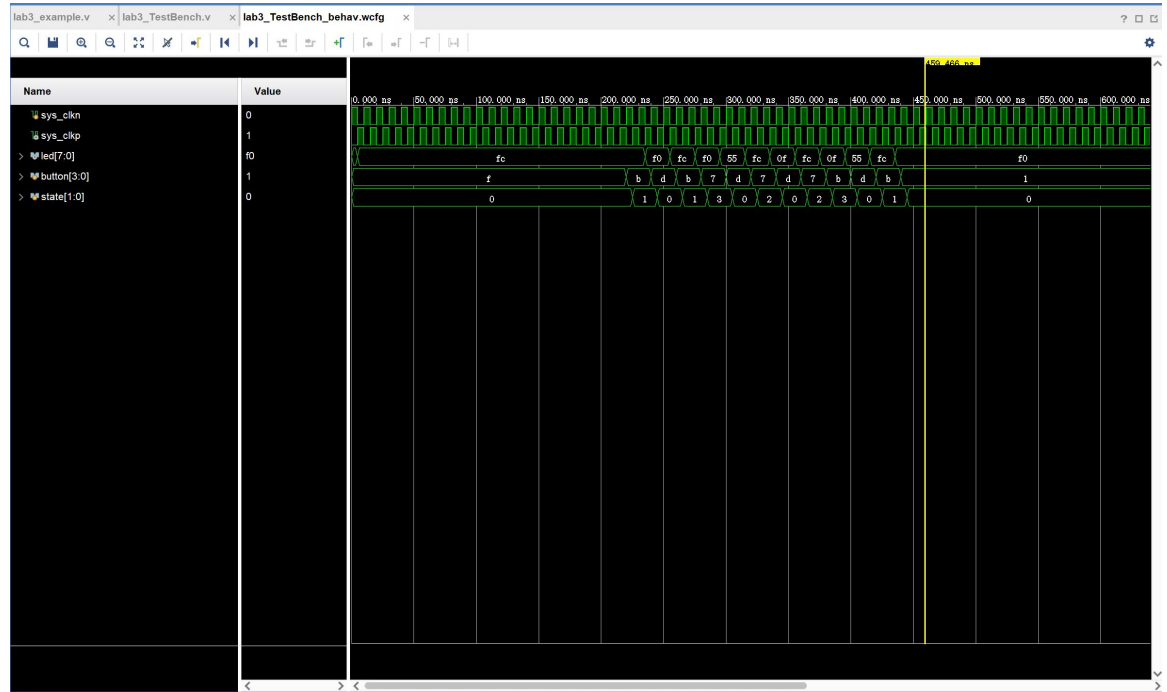


Lab3 Milestone 1 By E. Zhou & Q. Pang


Checkpoint 1.

(A) Screen
shot:




- (B) a. The led output (and there for led_register) is floating (undefined) initially and requires the first falling edge to become valid in the post implementation timing simulation while in behavior simulation it is valid immediately, this showcases signal setup time.
- b. All bits in the led output does not update at the same time, they change at different time due to different signal delays.
- c. Signals also does not update perfectly aligned with clock edges in post implementation timing sim, while signals edges aligned perfectly with clock edges in behavioral sim

Behavioral simulation:

 


Post implementation timing simulation:

 

- (C) It takes roughly 25ns for LEDs to change its output, there is some erroneous state between state transition, this is due to each bit of the leds output going through different amount of levels of combinational logic to be updated thus having different

delays, updating at different times.

 

- (D) It only takes 15 ns for behavioral sim to update, this is possibly due to that change the button is pressed right at the edge of clock, the FPGA might not be able to capture this change in button resulting the change being captured 1 clock cycle later (10ns) than behavioral sim where rising clock while perfectly capture everything.

Milestone2 Code:

FSM.V:

```
`timescale 1ns / 1ps
```

```
module FSM
```

```
    #( parameter one_sec = 100000000,
        half_sec = 50000000)
```

```
    (
    input wire clk,
    input wire[31:0] pedestrian,
    output wire[7:0] led
    );
```

```
    localparam STATE_Y1    = 3'd1;
    localparam STATE_G1    = 3'd2;
    localparam STATE_Y2    = 3'd3;
    localparam STATE_G2    = 3'd4;
    localparam STATE_PE1   = 3'd5;
    localparam STATE_PE2   = 3'd6;
```

```
    reg [3:0]    state = 0;
    reg [7:0]    led_register = 0; //R1, Y1, G1, R2, Y2, G2, R3, G3.
    reg [27:0]   counter = 0;
    reg          cross = 0;
    reg          pedestrain_reg = 1; // initialized to 1 to prevent USB set up triggering pedestrian
```

```
event
```

```
    assign led = ~led_register; //map led wire to led_register
```

```
    always @(posedge clk)
```

```
    begin
```

```
        pedestrain_reg <= pedestrian[0];
```

```
        if ((pedestrain_reg == 1'b0) && (pedestrian[0] == 1'b1))
```

```

begin
    cross <= 1'b1;
end

case (state)
    STATE_G1 : begin
        led_register <= 8'b00110010;
        if (counter >= one_sec)
            begin
                state <= STATE_Y1;
                counter <= 0;
            end
        else
            begin
                counter <= counter + 1;
            end
        end
    end
    STATE_Y1 : begin
        led_register <= 8'b01010010;
        if (counter >= half_sec && cross)
            begin
                state <= STATE_PE1;
                counter <= 0;
                cross <= 0;
            end
        else if (counter >= half_sec)
            begin
                state <= STATE_G2;
                counter <= 0;
            end
        else
            begin
                counter <= counter + 1;
            end
        end
    end
    STATE_G2 : begin
        led_register <= 8'b10000110;
        if (counter >= one_sec)
            begin
                state <= STATE_Y2;
                counter <= 0;
            end
        else
            begin

```

```

        counter <= counter + 1;
    end
end
STATE_Y2 : begin
led_register <= 8'b10001010;
    if (counter >= half_sec && cross)
    begin
        state <= STATE_PE2;
        counter <= 0;
        cross <= 0;
    end
    else if (counter >= half_sec)
    begin
        state <= STATE_G1;
        counter <= 0;
    end
    else
    begin
        counter <= counter + 1;
    end
end
STATE_PE1 : begin
    led_register <= 8'b10010001;
    if (counter >= one_sec)
    begin
        state <= STATE_G2;
        counter <= 0;
    end
    else
    begin
        counter <= counter + 1;
    end
end
STATE_PE2 : begin
    led_register <= 8'b10010001;
    if (counter >= one_sec)
    begin
        state <= STATE_G1;
        counter <= 0;
    end
    else
    begin
        counter <= counter + 1;
    end
end

```

```

        end
        default: state <= STATE_G1;
    endcase
end
endmodule

```

lab3_example.v:

```

`timescale 1ns / 1ps
module lab3_example(
    input wire  [4:0] okUH,
    output wire  [2:0] okHU,
    inout wire  [31:0] okUHU,
    inout wire  okAA,
    output [7:0] led,
    input sys_clk,
    input sys_clkp
);

    wire [31:0] pedestrian;
    wire okClk; //These are FrontPanel wires needed to IO communication
    wire [112:0] okHE; //These are FrontPanel wires needed to IO communication
    wire [64:0] okEH; //These are FrontPanel wires needed to IO communication
    wire clk;

    IBUFGDS osc_clk(
        .O(clk),
        .I(sys_clkp),
        .IB(sys_clk)
    );

    okHost hostIF (
        .okUH(okUH),
        .okHU(okHU),
        .okUHU(okUHU),
        .okClk(okClk),
        .okAA(okAA),
        .okHE(okHE),
        .okEH(okEH)
    );

```

```

localparam endPt_count = 1;
wire [endPt_count*65-1:0] okEHx;
okWireOR # (.N(endPt_count)) wireOR (okEH, okEHx);

okWireIn wire10 ( .okHE(okHE),
                  .ep_addr(8'h00),
                  .ep_dataout(pedestrian));

FSM FSM(.clk(clk),
        .pedestrian(pedestrian),
        .led(led));

endmodule

lab3_TestBench.v:

`timescale 1ns / 1ps

module lab3_TestBench();
    //Declare wires and registers that will interface with the module under test
    //Registers are initilized to known states. Wires cannot be initilized.
    reg clk = 1;
    wire [7:0] led;
    reg [31:0]button;

    //Invoke the module that we like to test
    FSM#(.one_sec(100),.half_sec(50)) ModuleUnderTest (.pedestrian(button),.led(led),.clk(clk));

    // Generate a clock signal. The clock will change its state every 5ns.
    //Remember that the test module takes sys_clkp and sys_clkn as input clock signals.
    //From these two signals a clock signal, clk, is derived.
    //The LVDS clock signal, sys_clkn, is always in the opposite state than sys_clkp.
    always begin
        #5 clk = ~clk;
    end

    initial begin
        #0 button <= 0;
        #4000 button <= 1;
        #500 button <= 0;
        #2000 button <= 1;
    end
end
endmodule

```